

NEC 304

STLD

Lecture 20
Sequential Circuits: Flip flops

Rajeev Pandey


Department Of ECE

rajeevvce2007@gmail.com

Overview

- ° Latches respond to trigger **levels** on control inputs
 - Example: If $G = 1$, input reflected at output
- ° Difficult to precisely time when to store data with latches
- ° **Flip flops** store data on a **rising** or **falling** trigger edge.
 - Example: control input transitions from $0 \rightarrow 1$, data input appears at output
 - Data remains stable in the flip flop until next rising edge.
- ° Different types of flip flops serve different functions
- ° Flip flops can be defined with **characteristic functions**.

D Latch

 

D	C	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q_0	Q'_0


S	R	C	Q	Q'	
0	0	1	Q_0	Q'_0	Store
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	1	1	Disallowed
X	X	0	Q_0	Q'_0	Store

- When C is high, D passes from input to output (Q)

Clocking Event

- ° What if the output only changed on a **C transition?**

Positive edge triggered

 

Master-Slave D Flip Flop

- ° Consider two latches combined together
- ° Only one C value active at a time
- ° Output changes on **falling** edge of the clock


 


Fig. 5-9 Master-Slave D Flip-Flop

D Flip-Flop

- ° Stores a value on the positive edge of **C**
- ° Input changes at other times have no effect on output

Positive edge triggered


 


D	C	Q	Q'
0	↑	0	1
1	↑	1	0
X	0	Q_0	Q'_0

D gets latched to Q on the rising edge of the clock.


Clocked D Flip-Flop

  - ° Stores a value on the positive edge of C
- ° Input changes at other times have no effect on output




Positive and Negative Edge D Flip-Flop

 - ° D flops can be triggered on positive or negative edge
- ° Bubble before **Clock (C)** input indicates **negative edge trigger**




(a) Positive-edge

 


(a) Negative-edge

Fig. 5-11 Graphic Symbol for Edge-Triggered D Flip-Flop

 


Lo-Hi edge

 

Hi-Lo edge

Positive Edge-Triggered J-K Flip-Flop

 

(a) Circuit diagram

(b) Graphic symbol

Fig. 5-12 JK Flip-Flop

°Created from D flop

°J sets

°K resets

° $J=K=1 \rightarrow$ invert output


J	K	CLK	Q	Q'	
0	$0\uparrow$			Q_0	Q_0'
0	$1\uparrow$			0	1
1	$0\uparrow$			1	0
1	$1\uparrow$		TOGGLE		

Clocked J-K Flip Flop

- Two data inputs, **J** and **K**
- J** \rightarrow set, **K** \rightarrow reset, if **J**=**K**=1 then toggle output




(a)

 


(b)


Positive Edge-Triggered T Flip-Flop

 

(a) From JK flip-flop

 

(b) From D flip-flop

 

(c) Graphic symbol

Fig. 5-13 T Flip-Flop

°Created from D flop

° $T=0 \rightarrow$ keep current


°K resets

° $T=1 \rightarrow$ invert current

T	C	Q	Q'	
\emptyset			Q_0	
\uparrow		TOGGLE		Q_0'

Asynchronous Inputs

 
- J, K are **synchronous inputs**
 - Effects on the output are synchronized with the *CLK* input.
- **Asynchronous inputs** operate independently of the synchronous inputs and clock
 - Set the FF to 1/0 states *at any time*.



$\overline{\text{PRESET}}$	$\overline{\text{CLEAR}}$	FF response
1	1	Clocked operation*
0	1	$Q = 1$ (regardless of CLK)
1	0	$Q = 0$ (regardless of CLK)
0	0	Not used

*Q will respond to J, K, and CLK

Asynchronous Inputs

 


(a)


Point	Operation
a	Synchronous toggle on \overline{NGT} of \overline{CLK}
b	Asynchronous set on $\overline{PRE} = 0$
c	Synchronous toggle
d	Synchronous toggle
e	Asynchronous clear on $\overline{CLR} = 0$
f	CLR over-rides the \overline{NGT} of \overline{CLK}
g	Synchronous toggle

(b)

Asynchronous Inputs

 

(a) Circuit diagram

 

(b) Graphic symbol

R	C	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0


(b) Function table

- Note reset signal (R) for D flip flop
- If $R = 0$, the output Q is cleared
- This event can occur at any time, regardless of the value of the CLK

Fig. 5-14 D Flip-Flop with Asynchronous Reset

Parallel Data Transfer

 - ° Flip flops store outputs from combinational logic
- ° Multiple flops can store a collection of data



*After occurrence of NGT

Summary

- ° **Flip flops are powerful storage elements**
 - They can be constructed from gates and latches!
- ° **D flip flop is simplest and most widely used**
- ° **Asynchronous inputs allow for clearing and presetting the flip flop output**
- ° **Multiple flops allow for data storage**
 - The basis of computer **memory!**
- ° **Combine storage and logic to make a computation circuit**
- ° **Next time: Analyzing sequential circuits.**